



## Quiz EL204

# Transistor Amplifiers

Lucas Monteiro Nogueira

### ►► PROBLEM DISTRIBUTION

| Problems | Subject                       |
|----------|-------------------------------|
| 1 – 4    | Common-source configurations  |
| 5 – 7    | Common-emitter configurations |
| 8 – 11   | Common-gate configurations    |
| 12 – 14  | Common-base configurations    |
| 15 – 20  | MOS cascode circuits          |
| 21 – 23  | BJT cascode circuits          |

### ►► PROBLEMS

#### ► Problem 1 (Sedra and Smith, 2015, w/ permission)

Calculate the overall voltage gain of a common-source amplifier that is fed a  $1.2\text{-M}\Omega$  source and connected to a  $15\text{-k}\Omega$  load. The MOSFET has transconductance  $g_m = 2\text{ mA/V}$ , and a drain resistance  $R_D = 10\text{ k}\Omega$  is utilized.

Related equation: eq. 1

#### ► Problem 2 (Sedra and Smith, 2015, w/ permission)

A MOSFET connected in the common-source configuration has a transconductance  $g_m = 5\text{ mA/V}$ . When a resistance  $R_s$  is connected in the source lead, the effective transconductance is reduced to  $2\text{ mA/V}$ . What do you estimate the value of  $R_s$  to be?

Related equation: eq. 2

#### ► Problem 3 (Sedra and Smith, 2015, w/ permission)

A common-source amplifier utilizes a MOSFET operated at overdrive voltage  $V_{OV} = 0.25\text{ V}$ . The amplifier feeds a load resistance  $R_L = 15\text{ k}\Omega$ . The designer selects a drain resistance  $R_D = 2R_L$ . If it is required to realize an overall voltage gain  $G_v$  of  $-10\text{ V/V}$ , what transconductance  $g_m$  is needed? Also specify the bias current  $I_D$ . If, to increase the output signal swing,  $R_D$  is reduced to  $R_D = R_L$ , what does  $G_v$  become?

Related equation: eq. 1

#### ► Problem 4 (Sedra and Smith, 2015, w/ permission)

The overall voltage gain of a CS amplifier with a resistance  $R_s = 0.5\text{ k}\Omega$  in the source lead was measured and found to be  $-10\text{ V/V}$ . When  $R_s$  was shorted, but the circuit operation remained linear, the gain doubled. What must the transconductance  $g_m$  be? What value of  $R_s$  is needed to obtain an overall voltage gain to  $-5\text{ V/V}$ ?

Related equation: eq. 2

#### ► Problem 5 (Sedra and Smith, 2015, w/ permission)

A common-emitter amplifier utilizes a BJT with  $\beta = 100$  biased at collector current  $I_C = 0.5\text{ mA}$  and has a collector resistance  $R_C = 12\text{ k}\Omega$  and is connected to an emitter lead resistance  $R_e = 250\text{ }\Omega$ . Find the input resistance  $R_{in}$ , the open-circuit voltage gain  $A_{vo}$ , and the output lead resistance  $R_o$ . If the amplifier is fed with a signal source having a resistance of  $10\text{ k}\Omega$ , and a load resistance  $R_L = 12\text{ k}\Omega$  is connected to the output terminal, find the resulting gain  $A_v$  with load resistance and the overall voltage gain  $G_v$ . If the peak voltage of the sine wave appearing between base and emitter is to be limited to  $5\text{ mV}$ , what signal amplitude  $\hat{v}_{sig}$  is allowed, and what output voltage signal appears across the load?

Related equations: eqs. 3, 4, and 5

► **Problem 6** (Sedra and Smith, 2015, w/ permission)

Inclusion of an emitter resistance  $R_e$  reduces the variability of the gain  $G_v$  due to the inevitable wide variance in the value of current gain parameter  $\beta$ . Consider a common-emitter amplifier operating between a signal source with resistance  $R_{sig} = 10 \text{ k}\Omega$  and a total collector resistance  $R_C || R_L$  of  $10 \text{ k}\Omega$ . The BJT is biased at collector current  $I_C = 1 \text{ mA}$  and its  $\beta$  is specified to be nominally 100 but can lie in the range of 50 to 150. First determine the nominal value and the range of overall voltage gain  $|G_v|$  without resistance  $R_e$ . Then select a value of  $R_e$  that will ensure that  $|G_v|$  be within  $\pm 20\%$  of its new nominal value. Specify the value of  $R_e$ , the new nominal value of  $|G_v|$ , and the expected range of  $|G_v|$ .

Related equation: eq. 5

► **Problem 7** (Sedra and Smith, 2015, w/ permission)

In this problem we investigate the effect of the inevitable variability of  $\beta$  on the realized gain of the common-emitter amplifier. For this purpose, we write the overall voltage gain in a modified form of equation 5,

$$|G_v| = \frac{R'_L}{\frac{R_{sig}}{\beta} + \frac{1}{g_m}}$$

where  $R'_L = R_L || R_C$ . Consider the case  $R'_L = 10 \text{ k}\Omega$  and  $R_{sig} = 10 \text{ k}\Omega$ , and let the BJT be biased at  $I_C = 1 \text{ mA}$ . The BJT has a nominal  $\beta$  of 100. Use  $25 \text{ mV}$  as the thermal voltage.

**Problem 7.1:** What is the nominal value of  $|G_v|$ ?

**Problem 7.2:** If  $\beta$  can be anywhere between 50 and 150, what is the corresponding range of  $|G_v|$ ?

**Problem 7.3:** If in a particular design, it is required to maintain  $|G_v|$  within  $\pm 20\%$  of its nominal value, what is the maximum allowable range of  $\beta$ ?

**Problem 7.4:** If it is not possible to restrict  $\beta$  to the range found in Problem 7.3, and the designer has to contend with  $\beta$  in the range 50 to 150, what value of bias current  $I_C$  would result in  $|G_v|$  falling in a range of  $\pm 20\%$  of a new nominal value? What is the nominal value of  $|G_v|$  in this case?

Related equation: eq. 5

► **Problem 8** (Razavi, 2008, w/ permission)

A common-gate amplifier using an NMOS transistor for which  $g_m = 2 \text{ mA/V}$  has a  $5\text{-k}\Omega$  drain resistance  $R_D$  and a  $5\text{-k}\Omega$  load resistance  $R_L$ . The amplifier is driven by a voltage source having a  $750\text{-}\Omega$  resistance. What is the input resistance of the amplifier? What is the overall voltage gain  $G_v$ ? By what factor must the bias current  $I_D$  of the MOSFET be changed so that input resistance  $R_{in}$  matches signal-source resistance  $R_{sig}$ ?

Related equation: eq. 6

► **Problem 9** (Sedra and Smith, 2015, w/ permission)

A common-gate amplifier when fed with a signal source having  $R_{sig} = 100 \text{ }\Omega$  is found to have an overall voltage gain of  $12 \text{ V/V}$ . When a  $100\text{-}\Omega$  resistance was added in series with the signal generator the overall voltage gain decreased to  $10 \text{ V/V}$ . What must the transconductance  $g_m$  of the MOSFET be? If the MOSFET is biased at  $I_D = 0.25 \text{ mA}$ , at what overdrive voltage must it be operating?

Related equation: eq. 6

► **Problem 10** (Sedra and Smith, 2015, w/ permission)

A common-gate amplifier operating with transconductance  $g_m = 2 \text{ mA/V}$  and transistor output resistance  $r_o = 20 \text{ k}\Omega$  is fed with a signal source having resistance  $R_s = 1 \text{ k}\Omega$  and is loaded in a resistance  $R_L = 20 \text{ k}\Omega$ . Find input resistance  $R_{in}$ , output resistance  $R_{out}$ , and the voltage gain  $v_o/v_{sig}$  (output voltage/signal voltage).

Related equations: eqs. 7 and 8

► **Problem 11** (Sedra and Smith, 2015, w/ permission)

A common-gate amplifier operating with transconductance  $g_m = 2$  mA/V and transistor output resistance  $r_o = 20$  k $\Omega$  is fed with a signal source having a Norton equivalent composed of a current signal  $i_{sig}$  and a signal source resistance  $R_s = 20$  k $\Omega$ . The amplifier is loaded in a resistance  $R_L = 20$  k $\Omega$ . Find the input resistance  $R_{in}$  and  $i_o/i_{sig}$ , where  $i_o$  is the current through the load  $R_L$ . If  $R_L$  increases by a factor of 10, by what percentage does the current gain change?

Related equation: eq. 7

► **Problem 12** (Sedra and Smith, 2015, w/ permission)

A common-base amplifier is operating with load resistance  $R_L = 10$  k $\Omega$ , collector resistance  $R_C = 10$  k $\Omega$ , and signal-source resistance  $R_{sig} = 50$   $\Omega$ . At what current  $I_C$  should the transistor be biased for the input resistance  $R_{in}$  to equal that of the signal source? What is the resulting overall voltage gain? Assume a common-base current gain  $\alpha \approx 1$ .

Related equation: eq. 8

► **Problem 13** (Sedra and Smith, 2015, w/ permission)

What value of load resistance  $R_L$  causes the input resistance of the common-base amplifier to be approximately double the value of emitter resistance  $r_e$ ?

Related equation: eq. 9

► **Problem 14** (Sedra and Smith, 2015, w/ permission)

Show that for a CB amplifier,

$$\frac{R_{out}}{r_e} \approx 1 + \frac{\beta(R_e/r_e)}{\beta + 1 + (R_e/r_e)}$$

Generate a table for output resistance  $R_{out}$  as a multiple of transistor emitter resistance  $r_e$  with entries for circuit emitter lead resistance  $R_e = 0, r_e, 2r_e, 10r_e, (\beta/2)r_e, \beta r_e,$  and  $1000r_e$ . Let  $\beta = 100$ .

Related equation: eq. 10

► **Problem 15** (Sedra and Smith, 2015, w/ permission)


Consider a MOS cascode amplifier for which the CS and CG transistors are identical and are biased to operate at bias current  $I_D = 0.15$  mA with overdrive voltage  $V_{OV} = 0.2$  V. Also let Early voltage  $V_A = 1.5$  V. Find  $A_{v1}, A_{v2},$  and  $A_v$  for two cases:

**Problem 5.1:**  $R_L = 10$  k $\Omega$

**Problem 5.2:**  $R_L = 150$  k $\Omega$

► **Problem 16** (Sedra and Smith, 2015, w/ permission)

Consider the cascode amplifier illustrated below with the dc component of the input,  $V_i = 0.7$  V,  $V_{G2} = 1.0$  V,  $V_{G3} = 0.8$  V,  $V_{G4} = 1.1$  V, and  $V_{DD} = 1.8$  V. If all devices are matched (i.e., such that conduction parameters  $k_{n1} = k_{n2} = k_{p3} = k_{p4}$ ) and have ideal threshold voltages  $|V_t|$  of 0.5 V, what is the overdrive voltage at which the transistors are operating? What is the allowable voltage range at the output?

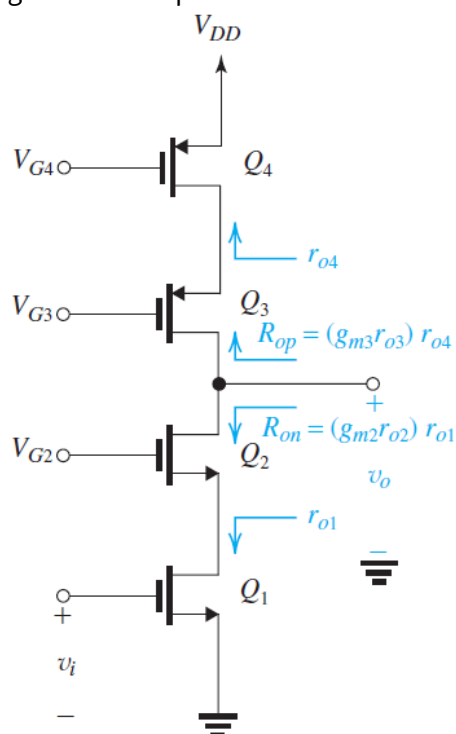

► **Problem 17** (Sedra and Smith, 2015, w/ permission)

Suppose the cascode amplifier illustrated in Problem 16 is operated at a current of 0.2 mA with all devices operating at an overdrive voltage  $|V_{ov}| = 0.2$  V. All devices have Early voltage  $|V_A| = 2$  V. Find  $g_{m1}$  (the transconductance of transistor  $Q_1$ ), the output resistance of the amplifier,  $R_{on}$ , and the output resistance of the current source,  $R_{op}$ . Also find the overall output resistance and the voltage gain realized.

► **Problem 18** (Sedra and Smith, 2015, w/ permission)


Reconsider the cascode amplifier introduced in Problem 16, taking  $V_i = 0.6$  V as the dc component of the input,  $V_{G2} = 0.9$  V,  $V_{G3} = 0.4$  V,  $V_{G4} = 0.7$  V, and  $V_{DD} = 1.3$  V. If all devices are matched, that is,  $k_{n1} = k_{n2} = k_{p3} = k_{p4}$ , and have equal ideal threshold voltage  $|V_t| = 0.4$  V, what is the overdrive voltage at which the four transistors are operating? What is the allowable voltage range at the output?

► **Problem 19** (Sedra and Smith, 2015, w/ permission)

Design the CMOS cascode amplifier illustrated in Problem 16 for the following specifications: transconductance  $g_{m1} = 1$  mA/V and voltage gain  $A_v = -280$  V/V. Assume that for the available fabrication process, Early voltage  $|V_A'| = 5$  V/ $\mu$ m for both NMOS and PMOS devices and process parameter  $\mu_n C_{ox} = 4\mu_p C_{ox} = 400$   $\mu$ A/V<sup>2</sup>. Use the same channel length  $L$  for all devices and operate all four devices at  $|V_{ov}| = 0.25$  V. Determine the required channel length  $L$ , the bias current  $I$ , and the aspect ratio  $W/L$  for each of the four transistors. Assume that suitable bias voltages have been chosen, and neglect the Early effect in determining the  $W/L$  ratios.


► **Problem 20** (Sedra and Smith, 2015, w/ permission)

A CMOS cascode amplifier such as the one illustrated below has identical common-source and common-gate transistors that have aspect ratio  $W/L = 5.4$   $\mu$ m/ $0.36$   $\mu$ m and are biased at  $I = 0.2$  mA. The fabrication process has process parameter  $\mu_n C_{ox} = 400$   $\mu$ A/V<sup>2</sup> and Early voltage  $V_A' = 5$  V/ $\mu$ m. At what value of load resistance  $R_L$  does the gain become  $-100$  V/V? What is the voltage gain of the common-source stage?

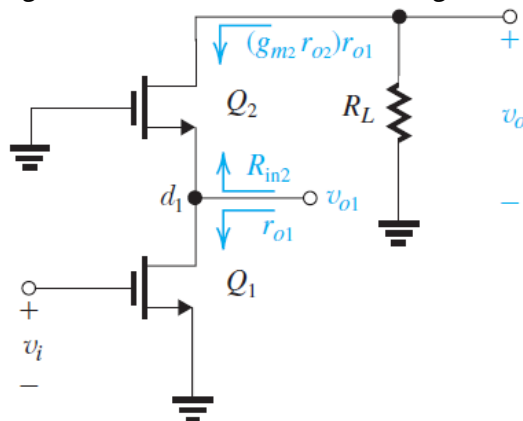

► **Problem 21**

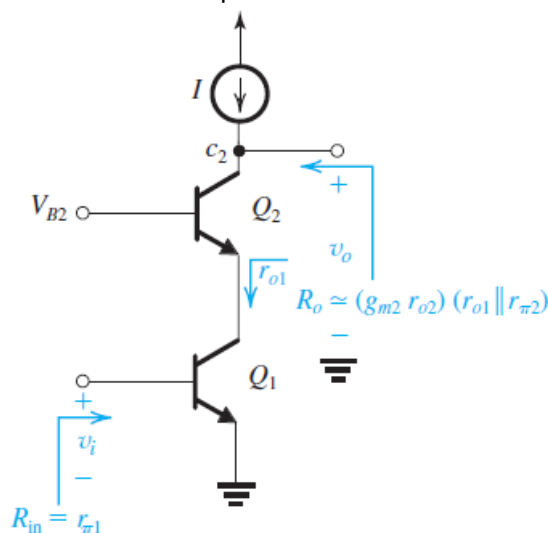A cascode current source formed of two *pnp* bipolar transistors for which current gain parameter  $\beta = 50$  and Early voltage  $V_A = 5$  V supplies a current of 0.2 mA. What is the output resistance?



## ► Problem 22


Consider the BJT cascode amplifier illustrated below when biased at a current of 0.2 mA.

**Problem 22.1:** Assuming that the *nnp* transistors have current gain parameter  $\beta = 100$  and Early voltage  $V_A = 5$  V, and that the *pnp* transistors have  $\beta = 50$  and  $|V_A| = 4$  V, find the output resistance of the amplifier,  $R_{on}$ , the output resistance of the current source,  $R_{op}$ , and the voltage gain,  $A_v$ .

**Problem 22.2:** Show that the maximum voltage gain achieved by the BJT cascode illustrated below is given by

$$|A_{v,\max}| = g_{m1} (\beta_2 r_{o2} \parallel \beta_3 r_{o3})$$

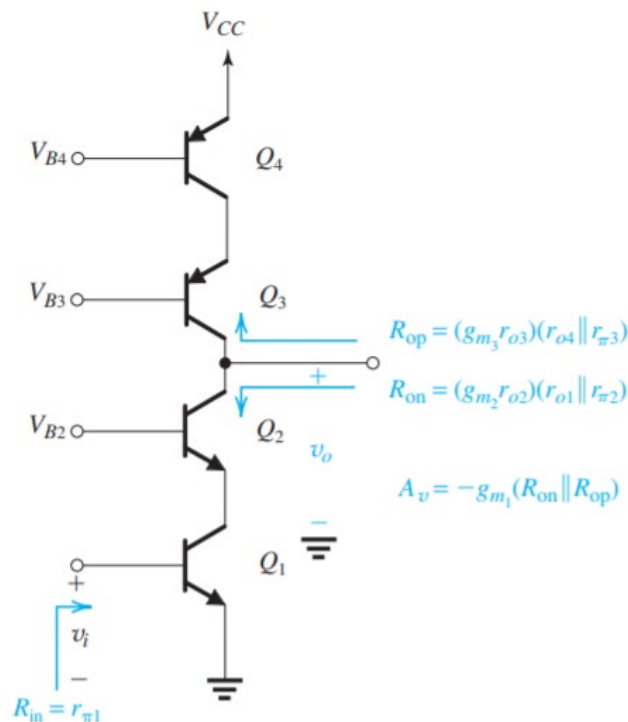Using this relationship, compute  $A_{v,\max}$  for the amplifier introduced in Problem 22.1.




## ► Problem 23

Consider the BJT cascode amplifier illustrated in Problem 22 for the case all transistors have equal current gain parameter  $\beta$  and transistor output resistance  $r_o$ . Show that the voltage gain  $A_v$  can be expressed in the form


$$A_v = -\frac{1}{2} \frac{|V_A|/V_T}{(V_T/|V_A|) + 1/\beta}$$

Evaluate  $A_v$  for the case  $|V_A| = 5$  V and  $\beta = 50$ . Note that except for the fact that  $\beta$  depends on  $I$  as a second-order effect, the gain is independent of the bias current  $I$ !

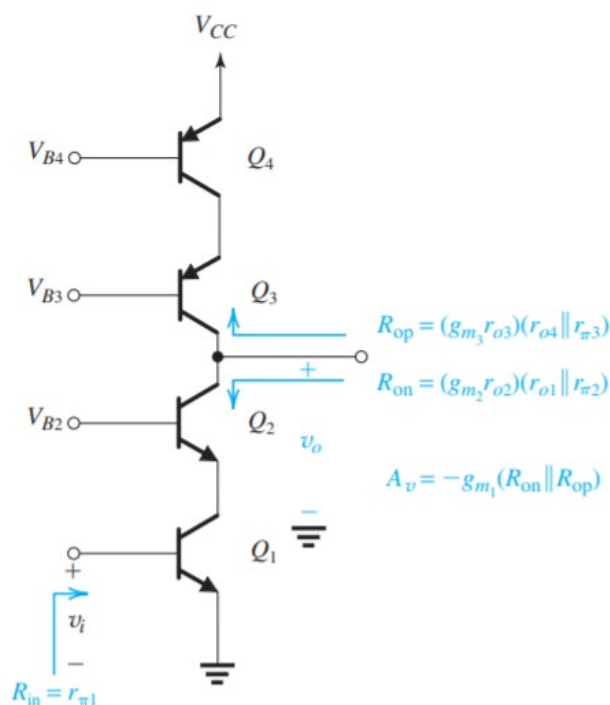

► **ADDITIONAL INFORMATION**

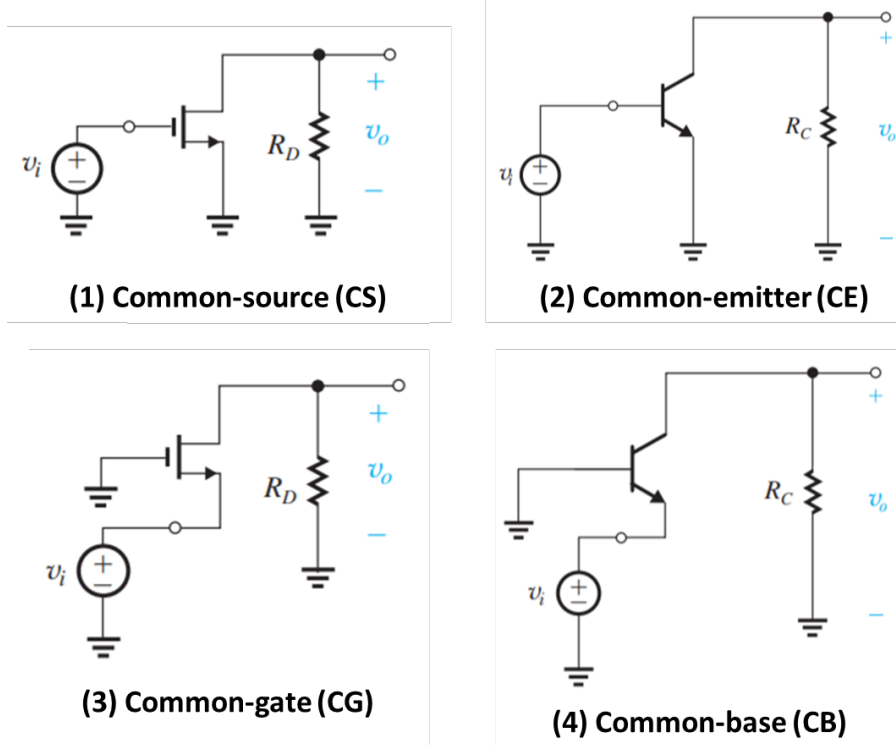**Figure 1** Basic transistor circuit configurations.

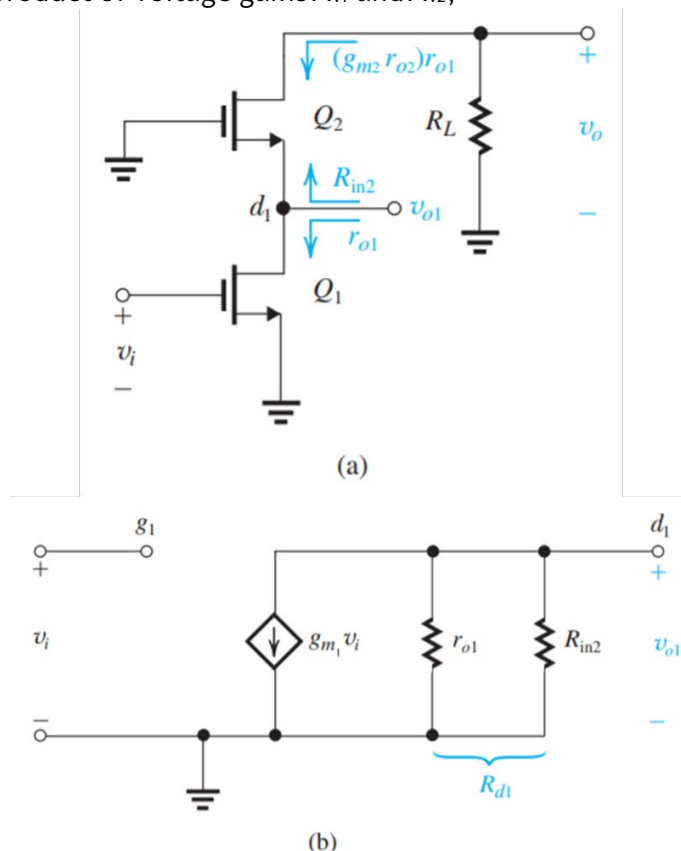


**Table 1** Gain distribution in the MOS cascode for various values of load resistance  $R_L$ .

| Case | $R_L$           | $R_{in2}$       | $R_{d1}$        | $A_{v1}$                | $A_{v2}$               | $A_v$                     |
|------|-----------------|-----------------|-----------------|-------------------------|------------------------|---------------------------|
| 1    | $\infty$        | $\infty$        | $r_o$           | $-g_m r_o$              | $g_m r_o$              | $-(g_m r_o)^2$            |
| 2    | $(g_m r_o) r_o$ | $r_o$           | $r_o/2$         | $-\frac{1}{2}(g_m r_o)$ | $g_m r_o$              | $-\frac{1}{2}(g_m r_o)^2$ |
| 3    | $r_o$           | $\frac{2}{g_m}$ | $\frac{2}{g_m}$ | $-2$                    | $\frac{1}{2}(g_m r_o)$ | $-(g_m r_o)$              |
| 4    | $0$             | $\frac{1}{g_m}$ | $\frac{1}{g_m}$ | $-1$                    | $0$                    | $0$                       |

**Notation:**

$R_L$  is the load resistance;  
 $R_{in2}$  is the input resistance of the CG transistor  $Q_2$ ;  
 $R_{d1}$  is the parallel resistance of  $r_{o1}$  (the transistor output resistance of  $Q_1$ ) and  $R_{in2}$  (the input resistance of  $Q_2$ );  
 $A_{v1}$  is the voltage gain of  $Q_1$ ;  
 $A_{v2}$  is the voltage gain of  $Q_2$ ;  
 $A_v$  is the product of voltage gains  $A_{v1}$  and  $A_{v2}$ ;



## Equations

1 → Overall voltage gain of a common-source amplifier

$$G_v = -g_m (R_D \parallel R_L)$$

**where**  $g_m$  is device transconductance,  $R_D$  is drain resistance, and  $R_L$  is load resistance.

2 → Voltage gain in a common-source amplifier with a resistance  $R_s$  connected to the source lead

$$G_{v(\text{with added source res.})} = -\frac{g_m (R_D \parallel R_L)}{1 + g_m R_s}$$

**where**  $g_m$  is device transconductance,  $R_D$  is drain resistance,  $R_L$  is load resistance, and  $R_s$  is the added source-lead resistance.

3 → Resistance-reflection rule

$$R_{in} = (1 + \beta)(r_e + R_e)$$

**where**  $\beta$  is the BJT current gain parameter,  $r_e$  is the emitter resistance, and  $R_e$  is the added emitter resistance.

4 → Open-circuit voltage gain in a common-emitter amplifier

$$A_{vo} = -\frac{g_m R_C}{1 + g_m R_e}$$

**where**  $g_m$  is transconductance parameter,  $R_C$  is collector resistance, and  $R_e$  is the added emitter resistance.

5 → Overall voltage gain in a common-emitter amplifier

$$G_v = -\beta \frac{R_C \parallel R_L}{R_{sig} + (1 + \beta)(r_e + R_e)}$$

**where**  $\beta$  is the BJT current gain parameter,  $R_C$  is collector resistance,  $R_L$  is load resistance,  $R_{sig}$  is the signal-source resistance,  $r_e$  is emitter resistance,  $R_e$  is added emitter resistance.

6 → Overall voltage gain in a common-gate amplifier

$$G_v = \frac{R_D \parallel R_L}{R_{sig} + \frac{1}{g_m}}$$

**where**  $R_D$  is drain resistance,  $R_L$  is load resistance,  $R_{sig}$  is signal-source resistance, and  $g_m$  is transconductance parameter.

7 → Input resistance in a common-gate amplifier

$$R_{in} = \frac{r_o + R_L}{1 + g_m r_o}$$

**where**  $r_o$  is transistor output resistance,  $R_L$  is load resistance, and  $g_m$  is transconductance parameter.

8 → Overall voltage gain in a common-base amplifier as a function of input resistance

$$G_v = \frac{R_{in}}{R_{in} + R_{sig}} g_m (R_C \parallel R_L)$$

**where**  $R_{in}$  is input resistance,  $R_{sig}$  is signal-source resistance,  $g_m$  is transconductance parameter,  $R_C$  is collector resistance, and  $R_L$  is load resistance.

9 → Input resistance in a common-base amplifier

$$R_{in} \approx r_e \frac{r_o + R_L}{r_o + \frac{R_L}{\beta + 1}}$$

**where**  $r_o$  is transistor output resistance,  $R_L$  is load resistance, and  $\beta$  is the BJT current gain parameter.

10 → Approximate output resistance in a common-gate amplifier

$$R_{out} \approx r_o \left[ 1 + g_m (R_e \parallel r_\pi) \right]$$

**where**  $r_o$  is transistor output resistance,  $g_m$  is transconductance parameter,  $R_e$  is added emitter resistance, and  $r_\pi$  is the internal base-emitter resistance.

## ► SOLUTIONS

### P.1 → Solution

The overall voltage gain  $G_v$  of a common-source amplifier is given by equation 1,

$$G_v = -g_m (R_D \parallel R_L) = -2.0 \times (10 \parallel 15) = -2.0 \times \left( \frac{10 \times 15}{10 + 15} \right) = \boxed{-12.0 \text{ V/V}}$$

### P.2 → Solution

Adding a resistance  $R_s$  to the source lead decreases the effective transconductance, and by extension the voltage gain, by a factor  $1 + g_m R_s$  (see equation 2). If  $g_{m1}$  is decreased to 2 mA/V from an initial  $g_m$  of 5 mA/V, the resistance connected to the source lead must be

$$\begin{aligned} g_{m1} &= \frac{g_m}{1 + g_m R_s} \rightarrow g_{m1} (1 + g_m R_s) = g_m \\ \therefore g_{m1} + g_{m1} g_m R_s &= g_m \\ \therefore R_s &= \frac{g_m - g_{m1}}{g_m g_{m1}} = \frac{5 - 2}{5 \times 2} = 0.3 \text{ k}\Omega = \boxed{300 \Omega} \end{aligned}$$

### P.3 → Solution

Noting that  $R_L = 15 \text{ k}\Omega$  and  $R_D = 2R_L = 30 \text{ k}\Omega$ , we can establish the required transconductance from the voltage gain  $G_v = -10$ ,

$$\begin{aligned} G_v = -g_m (R_D \parallel R_L) &= -10 \rightarrow g_m = \frac{10}{R_D \parallel R_L} \\ \therefore g_m &= \frac{10}{30 \parallel 15} = \frac{10}{\frac{30 \times 15}{30 + 15}} = \boxed{1.0 \text{ mA/V}} \end{aligned}$$

Referring to the definition of transconductance for a MOSFET, we write

$$\begin{aligned} g_m &= \frac{2I_D}{V_{OV}} \rightarrow I_D = \frac{g_m V_{OV}}{2} \\ \therefore I_D &= \frac{g_m V_{OV}}{2} = \frac{1.0 \times 0.25}{2} = \boxed{0.125 \text{ mA}} \end{aligned}$$

If drain resistance  $R_D$  is halved to 15 kΩ, the overall voltage gain becomes

$$G_v = -g_m (R_D \parallel R_L) = -1.0 \times (15 \parallel 15) = -1.0 \times 7.5 = \boxed{-7.5 \text{ V/V}}$$

### P.4 → Solution

The overall voltage gain of a CS amplifier in the presence of a source lead resistance is expressed as (equation 2)

$$G_{v(\text{with added source res.})} = -\frac{g_m (R_D \parallel R_L)}{1 + g_m R_s} \rightarrow -10 = -\frac{g_m (R_D \parallel R_L)}{1 + g_m \times 0.5} \quad (\text{I})$$

The overall voltage gain with no added source lead resistance is given by the now obvious relation

$$G_{v(\text{no added source res.})} = -g_m (R_D \parallel R_L) = 2G_{v(\text{with added source res.})} = -20 \text{ V}$$

Substituting in (I) and solving for transconductance,

$$\begin{aligned} -10 &= \frac{-20}{1 + 0.5g_m} \rightarrow -10 - 5g_m = -20 \\ \therefore g_m &= \frac{20 - 10}{5} = \boxed{2 \text{ mA/V}} \end{aligned}$$

Equipped with the value of  $g_m$ , the source lead resistance  $R_s$  needed to produce  $G_v = -16 \text{ V/V}$  easily follows,

$$\begin{aligned} -16 &= -\frac{g_m (R_D \parallel R_L)}{1 + g_m R_s} \rightarrow -16 = \frac{-20}{1 + 2R_s} \\ \therefore -16 - 32R_s &= -20 \end{aligned}$$



$$\therefore R_s = \frac{-20+16}{-32} = 0.125 \text{ k}\Omega = \boxed{125 \Omega}$$

### P.5 → Solution

The transconductance of the device is

$$g_m = \frac{I_C}{V_T} = \frac{0.5}{25 \times 10^{-3}} = 20 \text{ mA/V}$$

The emitter resistance is then

$$r_e = \frac{1}{g_m} = \frac{1}{20 \times 10^{-3}} = 50 \Omega$$

The input resistance is calculated to be (equation 3)

$$R_{in} = (1 + \beta)(r_e + R_e) = (1 + 100) \times (0.05 + 0.25) = \boxed{30.3 \text{ k}\Omega}$$

For this simple CE amplifier, the output resistance coincides with the collector resistance,

$$\boxed{R_C = 12 \text{ k}\Omega}$$

The open-circuit voltage gain is (equation 4)

$$A_{vo} = -\frac{g_m R_C}{1 + g_m R_e} = -\frac{(20 \times 10^{-3}) \times (12 \times 10^3)}{1 + (20 \times 10^{-3}) \times 250} = \boxed{-40 \text{ V/V}}$$

To determine the gain  $A_v$  with load resistance, we write

$$A_v = A_{vo} \left( \frac{R_L}{R_L + R_o} \right) = -40 \times \left( \frac{12}{12 + 12} \right) = \boxed{-20 \text{ V/V}}$$

As for the overall voltage gain  $G_v$  (equation 5),

$$G_v = -\beta \frac{R_C \parallel R_L}{R_{sig} + (1 + \beta)(r_e + R_e)} = -100 \times \frac{12 \parallel 12}{10 + (1 + 100) \times (0.05 + 0.25)} = \boxed{-14.9 \text{ V/V}}$$

If the peak voltage of the sine wave is to be no greater than 5 mV, the corresponding input signal voltage is, at most,

$$\frac{v_\pi}{v_i} = \frac{r_e}{r_e + R_e} \rightarrow v_i = \left( \frac{r_e + R_e}{r_e} \right) v_\pi$$

$$\therefore v_i = \left( \frac{0.05 + 0.25}{0.05} \right) \times 5 = 30 \text{ mV}$$

so that, for the allowable signal voltage amplitude  $\hat{v}_{sig}$ ,

$$\hat{v}_{sig} = \left( \frac{R_{in} + R_{sig}}{R_{in}} \right) v_i = \left( \frac{30.3 + 10}{30.3} \right) \times 30 = \boxed{39.9 \text{ mV}}$$

Lastly, the output voltage signal that appears across the load is

$$\hat{v}_o = \hat{v}_{sig} |G_v| = 39.9 \times 14.9 = 595 \text{ mV} = \boxed{0.595 \text{ V}}$$

### P.6 → Solution

Let us first state the usual relationship for overall current gain in a CE configuration (equation 5),

$$G_v = -\beta \frac{R_C \parallel R_L}{R_{sig} + (1 + \beta)(r_e + R_e)} = -\beta \frac{R_C \parallel R_L}{R_{sig} + (1 + \beta) \left( \frac{V_T}{I_E} + R_e \right)} \quad (I)$$

Emitter current  $I_E$  can be determined from the nominal common-base current gain  $\alpha$ , namely

$$\alpha = \frac{\beta}{\beta + 1} = \frac{100}{100 + 1} = 0.990$$

so that

$$I_E = \frac{I_C}{\alpha} = \frac{1.0}{0.990} = 1.01 \text{ mA}$$

The overall voltage gain with no added emitter resistance  $R_e$  is, substituting in (l),

$$G_v = -100 \times \frac{10 \times 10^3}{(10 \times 10^3) + (1 + 100) \times \left( \frac{25 \times 10^{-3}}{1.01 \times 10^{-3}} + 0 \right)} = -80 \text{ V/V}$$

Now, if  $\beta$  is set to vary between 50 and 150, the corresponding  $\alpha$  will vary from 0.98 to 0.99. Current  $I_E$  will attain a minimum value of

$$I_{E,\min} = \frac{I_C}{\alpha} = \frac{1.0}{0.990} = 1.01 \text{ mA}$$

and a maximum value of

$$I_{E,\max} = \frac{I_C}{\alpha} = \frac{1.0}{0.980} = 1.02 \text{ mA}$$

Taking  $\beta = 50$ , the nominal value of  $|G_v|$  without resistance  $R_e$  is

$$G_v = -50 \times \frac{10 \times 10^3}{(10 \times 10^3) + (1 + 50) \times \left( \frac{25 \times 10^{-3}}{1.02 \times 10^{-3}} + 0 \right)} = -44.4 \text{ V/V}$$

while for  $\beta = 150$ ,

$$G_v = -150 \times \frac{10 \times 10^3}{(10 \times 10^3) + (1 + 150) \times \left( \frac{25 \times 10^{-3}}{1.01 \times 10^{-3}} + 0 \right)} = -109 \text{ V/V}$$

Accordingly, with no added emitter resistance the absolute value of the overall current gain will lie in the interval [44.4, 109] V/V. Now, we aim to find an added emitter resistance  $R_e$  that will ensure that the  $|G_v|$  be within 20% of its new nominal value  $G_{v,\text{nom}}$ . At the lower limit, we set  $|G_v| = 0.8G_{v,\text{nom}}$  and write

$$|G_v| = 50 \times \frac{10 \times 10^3}{(10 \times 10^3) + (1 + 50) \times \left( \frac{25 \times 10^{-3}}{1.02 \times 10^{-3}} + R_e \right)} = 0.8G_{v,\text{nom}}$$

At the upper limit, with  $|G_v| = 1.2G_{v,\text{nom}}$ ,

$$|G_v| = 150 \times \frac{10 \times 10^3}{(10 \times 10^3) + (1 + 150) \times \left( \frac{25 \times 10^{-3}}{1.01 \times 10^{-3}} + R_e \right)} = 1.2G_{v,\text{nom}}$$

Dividing one equation by the other and solving for  $R_e$ ,

$$\frac{150 \times \frac{10 \times 10^3}{(10 \times 10^3) + 151 \times (24.8 + R_e)}}{50 \times \frac{10 \times 10^3}{(10 \times 10^3) + 51 \times (24.5 + R_e)}} = \frac{1.2 \cancel{G_{v,\text{nom}}}}{0.8 \cancel{G_{v,\text{nom}}}}$$

$$\therefore 3 \times \frac{(10 \times 10^3) + 51 \times (24.5 + R_e)}{(10 \times 10^3) + 151 \times (24.8 + R_e)} = 1.5$$

$$\therefore \frac{11,250 + 51R_e}{13,740 + 151R_e} = 0.5$$

$$\therefore 11,250 + 51R_e = 6870 + 75.5R_e$$

$$\therefore R_e = \frac{11,250 - 6870}{75.5 - 51} = \boxed{179 \Omega}$$

Substituting this  $R_e$  into (l) yields the nominal voltage gain

$$G_{v,\text{nom}} = -\beta \frac{R_C \parallel R_L}{R_{\text{sig}} + (1 + \beta)(r_e + R_e)} = -100 \times \frac{10 \times 10^3}{(10 \times 10^3) + (1 + 100) \times \left( \frac{25 \times 10^{-3}}{1.01 \times 10^{-3}} + 179 \right)} = \boxed{-32.7 \text{ V/V}}$$

Using the  $R_e$  obtained above, we can establish the expected range of  $G_v$ ,

$$G_v = -50 \times \frac{10 \times 10^3}{(10 \times 10^3) + (1 + 50) \times \left( \frac{25 \times 10^{-3}}{1.02 \times 10^{-3}} + 179 \right)} = -24.5 \text{ V/V}$$

$$G_v = -150 \times \frac{10 \times 10^3}{(10 \times 10^3) + (1 + 150) \times \left( \frac{25 \times 10^{-3}}{1.02 \times 10^{-3}} + 179 \right)} = -36.8 \text{ V/V}$$

The overall voltage gain is expected to vary between  $-36.8 \text{ V/V}$  and  $-24.5 \text{ V/V}$ .

### P.7 → Solution

**Problem 7.1:** The nominal value of  $G_v$  is that which corresponds to the device's nominal  $\beta$ , which is 100. Noting that  $g_m = I_C/V_T$  and substituting the pertaining variables into  $G_v$ , we obtain

$$|G_v| = \frac{10 \times 10^3}{\frac{10 \times 10^3}{100} + \frac{1}{\left( \frac{1.0 \times 10^{-3}}{25 \times 10^{-3}} \right)}} = \boxed{80 \text{ V/V}}$$

**Problem 7.2:** Assuming  $|G_v|$  is monotonically increasing with  $\beta \in [50, 150]$ , we have, at one end,

$$|G_v| = \frac{10 \times 10^3}{\frac{10 \times 10^3}{50} + \frac{1}{\left( \frac{1.0 \times 10^{-3}}{25 \times 10^{-3}} \right)}} = \boxed{44.44 \text{ V/V}}$$

while at the other,

$$|G_v| = \frac{10 \times 10^3}{\frac{10 \times 10^3}{150} + \frac{1}{\left( \frac{1.0 \times 10^{-3}}{25 \times 10^{-3}} \right)}} = \boxed{109.10 \text{ V/V}}$$

Thus, the overall voltage gain varies from about  $44 \text{ V/V}$  to about  $109 \text{ V/V}$  in the range of  $\beta$ -values considered.

**Problem 7.3:** The nominal value of  $G_v$  was calculated to be  $80 \text{ V/V}$ ; if the device is allowed to vary within  $\pm 20\%$  of this specification, we have  $G_{v,\min} = 64 \text{ V/V}$  and  $G_{v,\max} = 96 \text{ V/V}$ . In one extreme, the corresponding  $\beta$  is

$$|G_{v,\min}| = 64 = \frac{10 \times 10^3}{\frac{10 \times 10^3}{\beta} + \frac{1}{\left( \frac{1.0 \times 10^{-3}}{25 \times 10^{-3}} \right)}} \rightarrow 64 = \frac{10,000}{\frac{10,000}{\beta} + 25}$$

$$\therefore 64 \left( \frac{10,000}{\beta} + \frac{25\beta}{\beta} \right) = 10,000$$

$$\therefore 640,000 + 1600\beta = 10,000\beta$$

$$\therefore 640,000 = 8400\beta$$

$$\therefore \beta_{\min} = \frac{640,000}{8400} = 76.19$$

At the other extreme, using Mathematica to speed things up,

$$\text{In[48]:= Solve}\left[96 == \frac{10000.}{\frac{10000.}{\beta} + \frac{1}{1/25}}, \beta\right]$$

$$\text{Out[48]:=}\left\{\{\beta \rightarrow 126.316\}\right\}$$

That is,  $\beta_{\max} = 126.32$ . The allowable range of  $\beta$  is  $76.19 \leq \beta \leq 126.32$ .

**Problem 7.4:** Let the new nominal  $G_v$  be  $|G_v|_{\text{nom}}$ . With  $\beta = 50$  and  $|G_v| = 0.8|G_v|_{\text{nom}}$ , we write

$$\frac{10 \times 10^3}{\frac{10 \times 10^3}{50} + \frac{1}{\left(\frac{I_C}{25 \times 10^{-3}}\right)}} = 0.8 |G_v|_{\text{nom}} \quad (\text{I})$$

With  $\beta = 150$  and  $|G_v| = 1.2 |G_v|_{\text{nom}}$ , we have

$$\frac{10 \times 10^3}{\frac{10 \times 10^3}{150} + \frac{1}{\left(\frac{I_C}{25 \times 10^{-3}}\right)}} = 1.2 |G_v|_{\text{nom}} \quad (\text{II})$$

Dividing (II) by (I) and solving for bias current, we get

$$\frac{\frac{10 \times 10^3}{150} + \frac{1}{\left(\frac{I_C}{25 \times 10^{-3}}\right)}}{\frac{10 \times 10^3}{50} + \frac{1}{\left(\frac{I_C}{25 \times 10^{-3}}\right)}} = \frac{1.2 |G_v|_{\text{nom}}}{0.8 |G_v|_{\text{nom}}}$$

```
In[52]= Solve[ $\frac{1.2}{0.8} = \frac{\frac{10000.}{150} + \frac{25 \cdot 10^{-3}}{i_c}}{\frac{10000.}{50} + \frac{25 \cdot 10^{-3}}{i_c}}$ ,  $i_c$ ]
```

```
Out[52]= {{ $i_c \rightarrow 0.000125$ }}
```

That is, the bias current that would have  $|G_v|$  fall in a range of  $\pm 20\%$  of the new nominal value is  $I_C = 0.125$  mA. This new nominal voltage gain is

$$|G_v| = \frac{10 \times 10^3}{\frac{10 \times 10^3}{100} + \frac{1}{0.125}} = \boxed{33.33 \text{ V/V}}$$

### P.8 → Solution

The input resistance of a typical common-gate amplifier equals the reciprocal of the FET's transconductance:

$$R_{\text{in}} = \frac{1}{g_m} = \frac{1}{2.0 \times 10^{-3}} = \boxed{500 \Omega}$$

To determine the overall voltage gain, we apply equation 6,

$$G_v = \frac{R_D \parallel R_L}{R_{\text{sig}} + \frac{1}{g_m}} = \frac{5.0 \parallel 5.0}{0.75 + 0.5} = \frac{5.0 \times 5.0}{5.0 + 5.0} = \frac{2.5}{1.25} = \boxed{2 \text{ V/V}}$$

Now, using the definition of transconductance, we may write

$$g_m = \sqrt{2k_n' I_{D,1}} = 2.0 \times 10^{-3} \quad (\text{I})$$

For the signal-source resistance  $R_{\text{sig}}$  to match the input resistance  $R_{\text{in}}$ , we must have

$$R_{\text{sig}} = R_{\text{in}} = \frac{1}{g_m} \rightarrow g_m = \frac{1}{R_{\text{in}}} = \frac{1}{750}$$

$$\therefore \sqrt{2k_n' I_{D,2}} = \frac{1}{750} \quad (\text{II})$$

Dividing (II) by (I), we obtain the ratio

$$\sqrt{\frac{2k_n' I_{D,2}}{2k_n' I_{D,1}}} = \frac{\frac{1}{750}}{2.0 \times 10^{-3}} = \frac{\frac{1}{750}}{\frac{1}{500}} = \frac{2}{3}$$

$$\therefore \frac{I_{D,2}}{I_{D,1}} = \left(\frac{2}{3}\right)^2 = \frac{4}{9}$$

$$\therefore \boxed{I_{D,2} = \frac{4}{9} I_{D,1}}$$

That is, the bias current must be multiplied by a factor of four-ninths in order to have the input resistance  $R_{in}$  match the signal-source resistance  $R_{sig}$ .

### P.9 → Solution

Recall that the overall gain of a common-gate amplifier is expressed as (equation 6)

$$G_v = \frac{R_D \parallel R_C}{R_{sig} + \frac{1}{g_m}}$$

At first,  $R_{sig} = 100 \Omega$  and  $G_v = 12 \text{ V/V}$ , that is,

$$12 = \frac{R_D \parallel R_C}{100 + \frac{1}{g_m}} \quad (\text{I})$$

After  $100 \Omega$  of resistance is added in series to the signal generator,  $R'_{sig} = 200 \Omega$  and  $G'_v = 10 \text{ V/V}$ , so that

$$10 = \frac{R_D \parallel R_C}{200 + \frac{1}{g_m}} \quad (\text{II})$$

Dividing (I) by (II) and solving for transconductance,

$$\frac{12}{10} = \frac{\frac{\cancel{R_D \parallel R_C}}{100 + \frac{1}{g_m}}}{\frac{\cancel{R_D \parallel R_C}}{200 + \frac{1}{g_m}}} = \frac{200 + \frac{1}{g_m}}{100 + \frac{1}{g_m}}$$

$$\therefore 12 \times \left(100 + \frac{1}{g_m}\right) = 10 \times \left(200 + \frac{1}{g_m}\right)$$

$$\therefore 1200 + \frac{12}{g_m} = 2000 + \frac{10}{g_m}$$

$$\therefore \frac{2}{g_m} = 800$$

$$\therefore g_m = \frac{2}{800} = \frac{1}{400} \text{ A/V} = \frac{1000}{400} \text{ mA/V}$$

$$\therefore \boxed{g_m = 2.5 \text{ mA/V}}$$

If the FET is biased at  $I_D = 0.25 \text{ mA}$ , the overdrive voltage  $V_{OV}$  must be

$$g_m = \frac{2I_D}{V_{OV}} \rightarrow V_{OV} = \frac{2I_D}{g_m}$$

$$\therefore V_{OV} = \frac{2 \times 0.25}{2.5} = \boxed{0.2 \text{ V}}$$

### P.10 → Solution

The input resistance is given by equation 7,

$$R_{in} = \frac{r_o + R_L}{1 + g_m r_o} = \frac{(20 + 20) \times 10^3}{1 + (2.0 \times 10^{-3}) \times (20 \times 10^3)} = \boxed{976 \Omega}$$

The output resistance is, in turn (equation 8),

$$R_{\text{out}} = r_o + (1 + g_m r_o) R_s = (20 \times 10^3) + [1 + (2.0 \times 10^{-3}) \times (20 \times 10^3)] \times (1.0 \times 10^3) = 61,000 \Omega$$

$$\therefore \boxed{R_{\text{out}} = 61.0 \text{ k}\Omega}$$

Lastly, the voltage gain is

$$\frac{v_o}{v_{\text{sig}}} = \frac{R_L}{R_s + R_{\text{in}}} = \frac{20}{1.0 + 0.976} = \boxed{10.1 \text{ V/V}}$$

### P.11 → Solution

We have all the data needed to compute input resistance  $R_{\text{in}}$  (equation 7),

$$R_{\text{in}} = \frac{r_o + R_L}{1 + g_m r_o} = \frac{(20 + 20) \times 10^3}{1 + (2.0 \times 10^{-3}) \times (20 \times 10^3)} = \boxed{976 \Omega}$$

Now, current gain  $i_o/i_{\text{sig}}$  can be expressed as

$$\left( \frac{i_o}{i_{\text{sig}}} \right)_0 = \frac{R_s}{R_{\text{in}} + R_s} = \frac{20}{0.976 + 20} = 0.953 \text{ A/A}$$

Once the load resistance is increased to  $R'_L = 10R_L$ , the current gain becomes

$$\left( \frac{i_o}{i_{\text{sig}}} \right)_1 = \frac{R_s}{R'_{\text{in}} + R_s} = \frac{20 \times 10^3}{\frac{(20 + 200) \times 10^3}{1 + (2.0 \times 10^{-3}) \times (20 \times 10^3)} + 20 \times 10^3} = 0.788 \text{ A/A}$$

This amounts to a percentage change in current gain given by

$$\Delta = \frac{\left( \frac{i_o}{i_{\text{sig}}} \right)_1 - \left( \frac{i_o}{i_{\text{sig}}} \right)_0}{\left( \frac{i_o}{i_{\text{sig}}} \right)_0} \times 100\% = \frac{0.788 - 0.953}{0.953} \times 100\% = -17.3\%$$

### P.12 → Solution

First, note that the input resistance  $R_{\text{in}}$  of a common-base amp can be estimated as

$$R_{\text{in}} \approx \frac{1}{g_m}$$

For the input resistance  $R_{\text{in}}$  to equal the signal-source resistance  $R_{\text{sig}} = 50 \Omega$ , the transconductance must be

$$\frac{1}{g_m} = R_{\text{in}} = R_{\text{sig}} = 50 \rightarrow g_m = \frac{1}{50} = 20 \text{ mA/V}$$

Using the definition of  $g_m$  for a BJT, we establish the collector current

$$g_m = \frac{I_C}{V_T} \rightarrow I_C = g_m V_T$$

$$\therefore I_C = (20 \times 10^{-3}) \times (25 \times 10^{-3}) = 5.0 \times 10^{-4} \text{ A} = \boxed{0.5 \text{ mA}}$$

The overall voltage gain  $G_v$  is, in turn (equation 8),

$$G_v = \frac{R_{\text{in}}}{R_{\text{in}} + R_{\text{sig}}} g_m (R_C \parallel R_L) = \frac{50}{50 + 50} \times (20 \times 10^{-3}) \times [(10 \times 10^3) \parallel (10 \times 10^3)]$$

$$\therefore \boxed{G_v = 50 \text{ V/V}}$$

### P.13 → Solution

First, note that the input resistance of a CB configuration is related to load resistance  $R_L$  and other resistance components by the expression (equation 9)

$$R_{\text{in}} \approx r_e \frac{r_o + R_L}{r_o + \frac{R_L}{\beta + 1}}$$

Setting  $R_{\text{in}} = 2r_e$  and solving for  $R_L$ , we obtain

$$\begin{aligned}
\cancel{\frac{r_o + R_L}{R_L}} = 2 \cancel{\frac{R_L}{r_o + \frac{R_L}{\beta + 1}}} &\rightarrow r_o + R_L = 2 \left( r_o + \frac{R_L}{\beta + 1} \right) \\
\therefore r_o + R_L &= 2r_o + \frac{2R_L}{\beta + 1} \\
\therefore R_L - \frac{2R_L}{\beta + 1} &= r_o \\
\therefore \frac{R_L(\beta + 1) - 2R_L}{\beta + 1} &= r_o \\
\therefore R_L(\beta + 1) - 2R_L &= (\beta + 1)r_o \\
\therefore R_L(\beta - 1) &= (\beta + 1)r_o \\
\therefore R_L &= \left( \frac{\beta + 1}{\beta - 1} \right) r_o
\end{aligned}$$

Thus, if the load resistance were set to  $(\beta + 1)/(\beta - 1)$  times the transistor output resistance  $r_o$ , the input resistance  $R_{in}$  would become twice the emitter resistance  $r_e$ . With  $\beta = 50$ , for example, the load resistance would have to be  $51/49 \approx 1.04$  times the value of  $r_e$ .

### P.14 → Solution

Starting with the equation for output resistance  $R_{out}$  (equation 10), we write

$$\begin{aligned}
R_{out} &\approx r_o + g_m r_o (R_e \parallel r_\pi) \rightarrow R_{out} \approx r_o \left[ 1 + g_m (R_e \parallel r_\pi) \right] \\
\therefore R_{out} &= r_o \left( 1 + \frac{\beta}{r_\pi} \frac{R_e r_\pi}{R_e + r_\pi} \right) \\
\therefore R_{out} &= r_o \left( 1 + \frac{\beta R_e}{R_e + r_\pi} \right) \\
\therefore R_{out} &= r_o \left[ 1 + \frac{\beta R_e}{R_e + (\beta + 1)r_e} \right] \\
\therefore \frac{R_{out}}{r_o} &= \left( 1 + \frac{\beta R_e}{\beta r_e + r_e + R_e} \right) \\
\therefore \frac{R_{out}}{r_o} &= \left[ 1 + \frac{\beta (R_e/r_e)}{\beta + 1 + (R_e/r_e)} \right]
\end{aligned}$$

The desired relationship has been demonstrated. We proceed to tabulate values of  $R_{out}/r_o$  as a function of different emitter lead resistances  $R_e$ . One way to go is to apply Mathematica's *Table* function,

```
In[524]= SetPrecision[Table[1 +  $\frac{100. * r}{101 + r}$ , {r, {0, 1, 2, 10, 50, 100, 1000.}}], 3]
```

```
Out[524]= {1.00, 1.98, 2.94, 10.0, 34.1, 50.8, 91.8}
```

The results are tabulated below.

| $R_e$     | $R_{out}/r_o$ |
|-----------|---------------|
| 0         | 1.0           |
| $r_e$     | 1.98          |
| $2r_e$    | 2.94          |
| $10r_e$   | 10.0          |
| $50r_e$   | 34.1          |
| $100r_e$  | 50.8          |
| $1000r_e$ | 91.8          |

### P.15 → Solution

**Problem 5.1:** We first determine the transconductance  $g_m$ ,

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 0.15}{0.2} = 1.5 \text{ mA/V}$$

The transistor output resistance  $r_o$  is given by

$$r_o = \frac{|V_A|}{I_D} = \frac{1.5}{0.15 \times 10^{-3}} = 10 \text{ k}\Omega$$

Note that  $r_o = R_L = 10 \text{ k}\Omega$ ; referring to Table 1, the present system fits into MOS cascode amplifier case 3. The voltage gain of transistor  $Q_1$  is fixed as

$$A_{v1} = -2.0 \text{ V/V}$$

The voltage gain of  $Q_2$  is, in turn,

$$A_{v2} = \frac{1}{2} g_m r_o = -\frac{1}{2} \times (1.5 \times 10^{-3}) \times (10 \times 10^3) = \boxed{7.5 \text{ V/V}}$$

The overall gain can be expressed as the product of the voltage gains of  $Q_1$  and  $Q_2$ ,

$$A_v = A_{v1} A_{v2} = -2.0 \times 7.5 = \boxed{-15 \text{ V/V}}$$

**Problem 5.2:** Note that

$$(g_m r_o) r_o = (1.5 \times 10^{-3}) \times (10 \times 10^3) \times (10 \times 10^3) = 150 \text{ k}\Omega$$

which happens to be the value of  $R_L$ ; accordingly, we are now in gain distribution case 2. The voltage gain of  $Q_1$  then becomes

$$A_{v1} = -\frac{1}{2} (g_m r_o) = -\frac{1}{2} \times [(1.5 \times 10^{-3}) \times (10 \times 10^3)] = \boxed{-7.5 \text{ V/V}}$$

while the gain of  $Q_2$  is found as

$$A_{v2} = g_m r_o = (1.5 \times 10^{-3}) \times (10 \times 10^3) = \boxed{15 \text{ V/V}}$$

Lastly, the overall gain is

$$A_v = A_{v1} A_{v2} = -7.5 \times 15 = \boxed{-113 \text{ V/V}}$$

### P.16 → Solution

The overdrive voltage  $V_{OV}$  for a PMOS transistor is of course

$$V_{OV} = V_{SG} - V_t = V_S - V_G - V_t$$

With reference to transistor  $Q_4$ , we may write

$$V_{OV} = V_{DD} - V_{G,4} - V_t = 1.8 - 1.1 - 0.5 = \boxed{0.2 \text{ V}}$$

Now, the minimum output voltage is given by

$$V_{o,\min} = V_{D,1} + V_{OV} = (V_{G,2} - V_{GS,2}) + V_{OV} \quad (\text{I})$$

Noting that

$$V_{GS,1} = V_{GS,2} = V_{SG,3} = V_{SG,4} = V_{OV} + |V_t| = 0.2 + 0.5 = 0.7 \text{ V}$$

we can substitute in (I) to obtain

$$V_{o,\min} = V_{G,2} - V_{GS,2} + V_{OV} = 1.0 - 0.7 + 0.2 = \underline{0.5 \text{ V}}$$

In turn, the maximum output voltage is

$$V_{o,\max} = V_{DD} - V_t = 1.8 - 0.5 = \underline{1.3 \text{ V}}$$

The allowable voltage range at the output is  $0.5 \leq V_o \leq 1.3 \text{ V}$ .

### P.17 → Solution

To find the transconductance of the transistors, simply substitute the operating conditions  $I_D = 0.2 \text{ mA}$  and  $|V_{OV}| = 0.2 \text{ V}$  into the usual definition,

$$g_{m1} = \frac{2I_D}{V_{OV}} = \frac{2 \times 0.2}{0.2} = \boxed{2.0 \text{ mA/V}}$$

To establish the output resistance  $R_{on}$  of the amplifier, we first compute the transistor output resistance  $r_o$ , which is assumed to be the same for all four FETs,

$$r_o = \frac{|V_A|}{I_D} = \frac{2.0}{0.2 \times 10^{-3}} = 10 \text{ k}\Omega$$

Accordingly,

$$R_{on} = (g_{m1} r_{o1}) r_{o2} = (2.0 \times 10^{-3}) \times (10 \times 10^3) \times (10 \times 10^3) = \boxed{200 \text{ k}\Omega}$$

Likewise, the output resistance  $R_{op}$  of the current source is



$$R_{op} = (g_{m1}r_{o3})r_{o4} = (2.0 \times 10^{-3}) \times (10 \times 10^3) \times (10 \times 10^3) = \boxed{200 \text{ k}\Omega}$$

The overall output resistance is then

$$R_o = R_{on} \parallel R_{op} = \frac{200 \times 200}{200 + 200} = \boxed{100 \text{ k}\Omega}$$

Lastly, we compute the voltage gain realized by the cascode amp,

$$A_v = -g_{m1} (R_{on} \parallel R_{op}) = -(2.0 \times 10^{-3}) \times (100 \times 10^3) = \boxed{-200 \text{ V/V}}$$

### P.18 → Solution

To establish the overdrive voltage of transistor operation, simply subtract the threshold voltage,  $|V_t| = 0.4 \text{ V}$ , from the dc component of input voltage,  $V_I = 0.6 \text{ V}$ ,

$$V_{OV} = V_I - V_t = 0.6 - 0.4 = \boxed{0.2 \text{ V}}$$

Next, we determine the minimum output voltage on the basis of transistor  $Q_2$ ; that is,

$$V_{o,\min} = V_{S,2} + V_{OV,2} \quad (\text{I})$$

Here,  $V_{S,2}$  is given by

$$\begin{aligned} V_{S,2} &= V_{G,2} - V_{GS,2} = V_{G,2} - (V_{OV} + V_t) = V_{G,2} - V_{OV} - V_t \\ \therefore V_{S,2} &= 0.9 - 0.2 - 0.4 = 0.3 \text{ V} \end{aligned}$$

Substituting in (I),

$$V_{o,\min} = 0.3 + 0.2 = \underline{0.5 \text{ V}}$$

The *maximum* output voltage, in turn, is calculated on the basis of transistor  $Q_3$ ,

$$V_{o,\max} = V_{S,3} - V_{OV,3} \quad (\text{II})$$

To determine source voltage  $V_{S,3}$ , we write

$$\begin{aligned} V_{S,3} &= V_{G,3} + V_{GS,3} = V_{G,3} + (V_{OV} + V_t) \\ \therefore V_{S,3} &= 0.4 + 0.2 + 0.4 = 1.0 \text{ V} \end{aligned}$$

Substituting in (II),

$$V_{o,\max} = 1.0 - 0.2 = \underline{0.8 \text{ V}}$$

Thus, the output voltage range is  $V_o \in [0.5, 0.8] \text{ V}$ .

### P.19 → Solution

Using the specified gain  $A_v = -280 \text{ V/V}$  and transconductance  $g_{m1} = 1 \text{ mA/V}$ , we can estimate the circuit output resistance  $R_o$  of the cascode network,

$$\begin{aligned} A_v &= -g_m R_o \rightarrow R_o = -\frac{A_v}{g_{m1}} \\ \therefore R_o &= -\frac{(-280)}{1.0 \times 10^{-3}} = 280 \text{ k}\Omega \end{aligned}$$

Using  $R_o$ , we can determine the transistor output resistances  $r_o$ , which are assumed equal for the four transistors,

$$\begin{aligned} R_o &= [(g_{o2}r_{o2})r_{o1} \parallel (g_{o3}r_{o3})r_{o4}] = [(1.0 \times 10^{-3}) \times r_o^2] \parallel [(1.0 \times 10^{-3}) \times r_o^2] = 280 \times 10^3 \\ \therefore \frac{[(1.0 \times 10^{-3}) \times r_o^2] \times [(1.0 \times 10^{-3}) \times r_o^2]}{(1.0 \times 10^{-3}) \times r_o^2 + (1.0 \times 10^{-3}) \times r_o^2} &= 280 \times 10^3 \\ \therefore r_o &= \sqrt{\frac{280 \times 10^3}{5.0 \times 10^{-4}}} = 23.7 \text{ k}\Omega \end{aligned}$$

Now, recall that  $r_o$  for a FET can be expressed as

$$r_o = \frac{V_A}{I} = \frac{V'_A L}{I} \rightarrow L = \frac{r_o I}{V'_A}$$

In order to determine the channel length  $L$ , we require the bias current  $I$ ,

$$g_m = \frac{2I}{V_{OV}} \rightarrow I = \frac{g_m |V_{OV}|}{2}$$

$$\therefore I = \frac{(1.0 \times 10^{-3}) \times 0.25}{2} = \boxed{0.125 \text{ mA}}$$

Thus,

$$L = \frac{r_o I}{V'_A} = \frac{(23.7 \times 10^3) \times (0.125 \times 10^{-3})}{5.0 \times 10^6} = \boxed{0.593 \mu\text{m}}$$

Next, we write the usual relationship for bias current in a FET and solve for width-to-length ratio,

$$I = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 V_{OV}^2 \rightarrow \left(\frac{W}{L}\right)_1 = \frac{2I}{\mu_n C_{ox} V_{OV}^2}$$

$$\therefore \left(\frac{W}{L}\right)_1 = \frac{2 \times (0.125 \times 10^{-3})}{(400 \times 10^{-6}) \times 0.25^2} = \boxed{10}$$

The width-to-length ratio of the NMOS labeled as 2 is the same as that of  $Q_1$ ,

$$\left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_1 = 10$$

The width-to-length ratio of the PMOS transistors is, noting that  $\mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2$ ,

$$I = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_3 V_{OV}^2 \rightarrow \left(\frac{W}{L}\right)_3 = \frac{2I}{\mu_p C_{ox} V_{OV}^2}$$

$$\therefore \left(\frac{W}{L}\right)_3 = \frac{2 \times (0.125 \times 10^{-3})}{(100 \times 10^{-6}) \times 0.25^2} = \boxed{40}$$

Finally,

$$\left(\frac{W}{L}\right)_4 = \left(\frac{W}{L}\right)_3 = 40$$

### P.20 → Solution

The information given suffices for us to compute the transconductance  $g_{m2}$ ,

$$g_{m2} = \sqrt{2k_p \left(\frac{W}{L}\right) I_D} = \sqrt{2 \times (400 \times 10^{-6}) \times \frac{5.4}{0.36} \times (0.2 \times 10^{-3})} = 1.55 \text{ mA/V}$$

Also, the device has 0.36- $\mu\text{m}$  effective length, therefore  $V_A = 5 \times 0.36 = 1.8 \text{ V}$ . We proceed to determine the transistor output resistance  $r_o$ ,

$$r_o = \frac{V_A}{I_D} = \frac{1.8}{0.2 \times 10^{-3}} = 9 \text{ k}\Omega$$

and from there the circuit output resistance  $R_o$ ,

$$R_o = (g_{m2} r_{o2}) r_{o1} = (1.55 \times 10^{-3}) \times (9.0 \times 10^3) \times (9.0 \times 10^3) = 126 \text{ k}\Omega$$

Now, setting the voltage gain to  $-100 \text{ V/V}$ ,

$$A_v = -g_{m1} (R_o \parallel R_L) = -100 \rightarrow R_o \parallel R_L = \frac{100}{1.55 \times 10^{-3}}$$

$$\therefore \frac{(126 \times 10^3) R_L}{(126 \times 10^3) + R_L} = \frac{100}{\underbrace{1.55 \times 10^{-3}}_{=64.5 \times 10^3}}$$

$$\therefore (126 \times 10^3) R_L = (64.5 \times 10^3) \times [(126 \times 10^3) + R_L]$$

$$\therefore (126 \times 10^3) R_L = 8.13 \times 10^9 + (64.5 \times 10^3) R_L$$

$$\therefore R_L = \frac{8.13 \times 10^9}{126 \times 10^3 - 64.5 \times 10^3} = \boxed{132 \text{ k}\Omega}$$

The gain attained will equal  $-100$  V/V if the load resistance utilized is close to  $130$  k $\Omega$ . We finish by determining the voltage gain of the CS amplifier,

$$A_v = g_m r_o = (1.55 \times 10^{-3}) \times (9.0 \times 10^3) = \boxed{14.0 \text{ V/V}}$$

### P.21 → Solution

The output resistance of a BJT cascode is given by

$$R_o \approx (g_{m2} r_{o2})(r_{o1} \parallel r_{\pi 2})$$

Before proceeding, we need the transconductance  $g_m$ , the transistor output resistance  $r_o$ , and the input resistance  $r_{\pi}$ . The value of  $g_m$  is

$$g_m = \frac{I}{V_T} = \frac{0.2 \times 10^{-3}}{0.025} = 8 \text{ mA/V}$$

The value of  $r_o$  is

$$r_o = \frac{V_A}{I} = \frac{5.0}{0.2 \times 10^{-3}} = 25 \text{ k}\Omega$$

The value of  $r_{\pi}$  is

$$r_{\pi} = \frac{\beta}{g_m} = \frac{50}{8.0 \times 10^{-3}} = 6.25 \text{ k}\Omega$$

Using our results, the value of  $R_o$  is calculated to be

$$R_o = \left[ (8.0 \times 10^{-3}) \times (25 \times 10^3) \right] \times (25 \times 10^3 \parallel 6.25 \times 10^3)$$

$$\therefore R_o = 200 \times \frac{(25 \times 10^3) \times (6.25 \times 10^3)}{(25 \times 10^3) + (6.25 \times 10^3)} = 1.0 \times 10^6 \Omega = \boxed{1.0 \text{ M}\Omega}$$

### P.22 → Solution

**Problem 22.1:** The output resistance  $R_{on}$  of the amplifier is given by

$$R_{on} = (g_{m2} r_{o2})(r_{o1} \parallel r_{\pi 2}) \quad (\text{I})$$

where subscripts 1 and 2 refer to the  $n$ pn transistors in the cascode. Transconductance  $g_{m2}$  is

$$g_{m2} = \frac{I_C}{V_T} = \frac{0.2 \times 10^{-3}}{25 \times 10^{-3}} = 8.0 \text{ mA/V}$$

The transistor output resistance  $r_{o1} = r_{o2}$  is

$$r_{o1} = r_{o2} = \frac{V_A}{I_C} = \frac{5.0}{0.2 \times 10^{-3}} = 25 \text{ k}\Omega$$

Input resistance  $r_{\pi 2}$  is

$$r_{\pi 2} = \frac{\beta_2}{g_{m2}} = \frac{100}{8.0 \times 10^{-3}} = 12.5 \text{ k}\Omega$$

Substituting in (I), we get

$$R_{on} = \left[ (8.0 \times 10^{-3}) \times (25 \times 10^3) \right] \times \left[ (25 \times 10^3) \parallel (12.5 \times 10^3) \right]$$

$$\therefore R_{on} = 200 \times \frac{(25 \times 10^3) \times (12.5 \times 10^3)}{(25 \times 10^3) + (12.5 \times 10^3)} = \boxed{1.67 \text{ M}\Omega}$$

The output resistance  $R_{op}$  of the current source is stated by the similar formula

$$R_{op} = (g_{m3} r_{o3})(r_{o4} \parallel r_{\pi 3}) \quad (\text{II})$$

Here, transconductance  $g_{m3}$  is

$$g_{m3} = \frac{I_C}{V_T} = \frac{0.2 \times 10^{-3}}{25 \times 10^{-3}} = 8.0 \text{ mA/V}$$

The transistor output resistance  $r_{o3} = r_{o4}$  is

$$r_{o3} = r_{o4} = \frac{V_A}{I_C} = \frac{4.0}{0.2 \times 10^{-3}} = 20 \text{ k}\Omega$$

Input resistance  $r_{\pi 3}$  is

$$r_{\pi 3} = \frac{\beta_3}{g_{m3}} = \frac{50}{8.0 \times 10^{-3}} = 6.25 \text{ k}\Omega$$

Substituting in (II), we get

$$R_{op} = \left[ (8.0 \times 10^{-3}) \times (20 \times 10^3) \right] \times \left[ (20 \times 10^3) \parallel (6.25 \times 10^3) \right]$$

$$\therefore R_{op} = 200 \times \frac{(20 \times 10^3) \times (6.25 \times 10^3)}{(20 \times 10^3) + (6.25 \times 10^3)} = \boxed{762 \text{ k}\Omega}$$

We proceed to compute voltage gain  $A_v$ ,

$$A_v = -g_{m1} (R_{on} \parallel R_{op}) = -8.0 \times (1670 \parallel 762)$$

$$\therefore A_v = -8.0 \times \frac{1670 \times 762}{1670 + 762} = \boxed{-4190 \text{ V/V}}$$

**Problem 22.2:** To show the relationship posited in the problem statement, we write, using the definitions of  $R_{on}$  and  $R_{op}$  for a BJT cascode amp,

$$A_v = -g_{m1} (R_{on} \parallel R_{op}) = -g_{m1} \left\{ \left[ (g_{m2} r_{o2}) (r_{o1} \parallel r_{\pi 2}) \right] \parallel \left[ (g_{m3} r_{o3}) (r_{o4} \parallel r_{\pi 3}) \right] \right\}$$

Here,  $r_{o4} \parallel r_{\pi 3} \rightarrow r_{\pi 3}$  because  $r_{o4} \gg r_{\pi 3}$  and  $r_{o1} \parallel r_{\pi 2} \rightarrow r_{\pi 2}$  because  $r_{o1} \gg r_{\pi 2}$ , giving

$$A_v = -g_{m1} \left\{ \left[ (g_{m2} r_{o2}) r_{\pi 2} \right] \parallel \left[ (g_{m3} r_{o3}) r_{\pi 3} \right] \right\}$$

$$\therefore A_v = -g_{m1} \left\{ \left[ (g_{m2} r_{\pi 2}) r_{o2} \right] \parallel \left[ (g_{m3} r_{\pi 3}) r_{o3} \right] \right\}$$

Note that the products in parentheses  $g_{m2} r_{\pi 2} = \beta_2$  and  $g_{m3} r_{\pi 3} = \beta_3$ , hence

$$|A_{v,\max}| = -g_{m1} (\beta_2 r_{o2} \parallel \beta_3 r_{o3})$$

as we intended to show.

In the case at hand,  $g_{m1} = g_{m2} = 8.0 \text{ mA/V}$ ,  $\beta_2 = 100$ ,  $r_{o2} = 25 \text{ k}\Omega$ ,  $\beta_3 = 50$ , and  $r_{o3} = 20 \text{ k}\Omega$ , so that

$$|A_{v,\max}| = -(8.0 \times 10^{-3}) \times \left\{ \left[ 100 \times (25 \times 10^3) \right] \parallel \left[ 50 \times (20 \times 10^3) \right] \right\}$$

$$\therefore |A_{v,\max}| = -(8.0 \times 10^{-3}) \times \left[ (2.5 \times 10^6) \parallel (1.0 \times 10^6) \right]$$

$$\therefore |A_{v,\max}| = -(8.0 \times 10^{-3}) \times \frac{(2.5 \times 10^6) \times (1.0 \times 10^6)}{(2.5 \times 10^6) + (1.0 \times 10^6)} = \boxed{-5710 \text{ V/V}}$$

### P.23 → Solution

The voltage gain of a BJT cascode is given by

$$A_v = -g_m (R_{on} \parallel R_{op}) \quad \text{(I)}$$

Here, the output resistance  $R_{on}$  of the amplifier and the output resistance  $R_{op}$  of the current source are given by

$$R_{on} = (g_{m2} r_{o2}) (r_{o1} \parallel r_{\pi 2}) = (g_m r_o) (r_o \parallel r_{\pi})$$

$$R_{op} = (g_{m3} r_{o3}) (r_{o4} \parallel r_{\pi 3}) = (g_m r_o) (r_o \parallel r_{\pi})$$

$$\therefore R_{on} = R_{op} = (g_m r_o) \times \frac{r_o \times r_{\pi}}{r_o + r_{\pi}} = \frac{I_C}{V_T} \times \frac{|V_A|}{I_C} \times \frac{I_C}{\frac{|V_A|}{I_C} + \frac{\beta V_T}{I_C}}$$

$$\therefore R_{on} = R_{op} = \frac{|V_A|}{\cancel{I_C}} \times \frac{|V_A| \beta \cancel{I_C}}{I_C (|V_A| + \beta V_T)} = \frac{\beta |V_A|^2}{I_C (|V_A| + \beta V_T)}$$

$$\therefore R_{on} = R_{op} = \frac{\beta |V_A|^2}{I_C \beta |V_A| \left( \frac{1}{\beta} + \frac{V_T}{|V_A|} \right)} = \frac{|V_A|}{I_C \left( \frac{V_T}{|V_A|} + \frac{1}{\beta} \right)}$$

Substituting in (I), we get

$$A_v = -g_m (R_{on} \parallel R_{op}) = -\frac{I_C}{V_T} \times \left\{ \left[ \frac{|V_A|}{I_C \left( \frac{V_T}{|V_A|} + \frac{1}{\beta} \right)} \right] \parallel \left[ \frac{|V_A|}{I_C \left( \frac{V_T}{|V_A|} + \frac{1}{\beta} \right)} \right] \right\}$$

$$\therefore A_v = -\frac{\cancel{I_C}}{V_T} \times \frac{|V_A|}{2 \cancel{I_C} \left( \frac{V_T}{|V_A|} + \frac{1}{\beta} \right)} = \boxed{-\frac{1}{2} \frac{|V_A|/V_T}{(V_T/|V_A|) + 1/\beta}}$$

Substituting  $|V_A| = 5 \text{ V}$  and  $\beta = 50$  brings to

$$\therefore A_v = -\frac{1}{2} \frac{5.0/0.025}{(0.025/5.0) + 1/50} = \boxed{-4000 \text{ V/V}}$$

## ▶ REFERENCE

- SEDRA, A.S. and SMITH, K.C. (2015). *Microelectronic Circuits*. 7th edition. Oxford: Oxford University Press.



Was this material helpful to you? If so, please consider donating a small amount to our project at [www.montoguequiz.com/donate](http://www.montoguequiz.com/donate) so we can keep posting free, high-quality materials like this one on a regular basis.